

Signals and Systems - MAE 143A
Midterm Exam - Winter Quarter 2008

Student name and number _____

For all the questions you need to show ALL your work to get to the answer.

1. (10 points) The circuit in Figure 1 (left graph) represents a “practical passive filter”. The circuit is excited by a voltage difference $U(t)$ and has a response of $V(t)$. Determine:
- (i) A model of the circuit in the form of a second-order ODE. *Hint:* Take derivatives with respect to time in the capacitor law and combine it with the inductor law.
 - (ii) The state-space representation of the system. Write the state-space model in matrix form.

Solution:

(i) An ODE model for this system can be found using the the KVL and circuit element laws. Let i be the current going through the resistor, inductor and capacitor. Let V_R , V_L and V_C be the voltage differences across R , L , and C , respectively.

By the KCL, we have that $i_R = i_C = i_L$.

By the KVL, we have that:

$$U - V_R - V_L - V_C = 0, \quad \text{using KVL for the marked loop,} \quad (1)$$

$$V_C - V = 0, \quad \text{using also KVL for the loop with } C \text{ and } V \quad (2)$$

The circuit element laws are given by:

$$V_R = iR, \quad (3)$$

$$L \frac{di}{dt} = V_L \iff \frac{di}{dt} = \frac{1}{L} V_L \quad (4)$$

$$i = C \frac{dV_C}{dt}, \quad (5)$$

By equation (2), we have that $V_C = V$. Since everything has to be expressed in terms of V , we differentiate with respect to time in equation (5). Putting this together with equation (4), we obtain V_L in terms of the second derivative of V :

$$\begin{cases} \frac{di}{dt} = C \frac{d^2V}{dt^2} \\ \frac{di}{dt} = \frac{1}{L} V_L \end{cases} \implies V_L = LC \frac{d^2V}{dt^2}$$

On the other hand, (3) and (5) give that $V_R = CR \frac{dV}{dt}$. Now, using equation (1), and substituting the obtained values of V_L and V_R , we have that:

$$U = CR \frac{dV}{dt} + LC \frac{d^2V}{dt^2} + V \quad (6)$$

(ii) There is only one unknown in the system and that is the response V . Since the ODE is second order, the state dimension will be 2. Let us denote by $\mathbf{x} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$ the state vector variable. We have that:

$$x_1 = V, \quad x_2 = \dot{V}.$$

Then, $\dot{x}_1 = \dot{x}_2$ and, using equation (6), $\dot{x}_2 = -\frac{1}{LC}V - \frac{CR}{LC}\dot{V} - \frac{1}{LC}U$. From here we have:

$$\begin{aligned} \dot{x}_1 &= x_2, \\ \dot{x}_2 &= -\frac{1}{LC}x_1 - \frac{R}{L}x_2 - \frac{1}{LC}U, \end{aligned}$$

or, in matrix form:

$$\dot{\mathbf{x}} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \mathbf{x} + \begin{bmatrix} 0 \\ -\frac{1}{LC} \end{bmatrix} U = \mathbf{A} \mathbf{x} + \mathbf{B} U.$$

2. (7 points) Let $U(t)$ be a periodic signal defined for all $t \in \mathbb{R}$ with fundamental period $T = 4$. For $t \in [0, 4]$ the signal is graphed in Figure 1 (right).

(i) Describe this signal for $t > 0$ as an infinite sum of shifted and amplified unit step functions.

(ii) Suppose that the zero-state response of the circuit system to the unit step function $1(t)$ is

$$V(t) = \frac{1}{14}e^{-\frac{t}{2}} + \frac{1}{7}, \quad \text{for } t > 0,$$

for certain values of R, L, C . Determine the circuit system response $W(t)$ to this $U(t)$ from an initial condition at the zero state. Justify your answer based on the system properties.

Solution: (i) The periodic signal of the figure, can be described as the following infinite sum:

$$\begin{aligned} U(t) &= 7 \cdot 1(t-1) - 2 \cdot 1(t-2) - 5 \cdot 1(t-4) \\ &\quad + 7 \cdot 1(t-5) - 2 \cdot 1(t-6) - 5 \cdot 1(t-8) \\ &\quad + 7 \cdot 1(t-9) - 2 \cdot 1(t-10) - 5 \cdot 1(t-12) \dots \end{aligned}$$

or in a compact formula as:

$$U(t) = \sum_{k=0}^{+\infty} 7 \cdot 1(t - (4k + 1)) - 2 \cdot 1(t - (4k + 2)) - 5 \cdot 1(t - (4k + 4)).$$

(ii) Because the state space representation of the circuit can be written in the form $\dot{\mathbf{x}} = \mathbf{A} \mathbf{x} + \mathbf{B} U$ for constant matrices \mathbf{A} and \mathbf{B} , the system is LTI. Therefore, the system response to the input $U(t)$ can be obtained as a sum of the following responses:

Input	→	Output
$7 \cdot 1(t - 4k - 1)$	→	$7 \cdot V(t - 4k - 1),$
$-2 \cdot 1(t - 4k - 2)$	→	$-2 \cdot V(t - 4k - 2),$
$-5 \cdot 1(t - 4k - 3)$	→	$-5 \cdot V(t - 4k - 4).$

Using the expression of $V(t) = \left(\frac{1}{14}e^{-\frac{t}{2}} + \frac{1}{7}\right) 1(t)$ we get:

$$\begin{aligned} 7 \cdot V(t - 4k - 1) &= \left(\frac{1}{2}e^{-\frac{t-4k-1}{2}} + 1\right) 1(t - 4k - 1), \\ -2 \cdot V(t - 4k - 2) &= -\left(\frac{1}{7}e^{-\frac{t-4k-2}{2}} + \frac{2}{7}\right) 1(t - 4k - 2), \\ -5 \cdot V(t - 4k - 4) &= -\left(\frac{5}{14}e^{-\frac{t-4k-4}{2}} + \frac{5}{7}\right) 1(t - 4k - 4). \end{aligned}$$

In this way, the overall response of the system to $U(t)$ will be:

$$\begin{aligned} W(t) &= \sum_{k=0}^{+\infty} \left(\frac{1}{2}e^{-\frac{t-4k-1}{2}} + 1\right) 1(t - 4k - 1) - \left(\frac{1}{7}e^{-\frac{t-4k-2}{2}} + \frac{2}{7}\right) 1(t - 4k - 2) \\ &\quad - \left(\frac{5}{14}e^{-\frac{t-4k-4}{2}} + \frac{5}{7}\right) 1(t - 4k - 4). \end{aligned}$$

3. (8 points) Suppose a system is modeled by

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & \sqrt{8} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} u.$$

Determine the zero-input response of the system to any initial condition $x_1(0) = C$, $x_2(0) = D$. Does the zero-input response satisfy the conditions for BIBO stability?

Solution: The zero-input response of the system is the solution to the homogeneous equation

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & \sqrt{8} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

with initial conditions $x_1(0) = C$ and $x_2(0) = D$. The solution of the ODE has the form $x_1(t) = K_1 e^{\lambda_1 t} + K_2 e^{\lambda_2 t}$, where λ_1, λ_2 are the solutions to $\det(\lambda I_2 - \mathbf{A}) = 0$. That is,

$$\det \begin{bmatrix} \lambda & -1 \\ 1 & \lambda - \sqrt{8} \end{bmatrix} = 0, \quad \iff \quad \lambda(\lambda - \sqrt{8}) + 1 = 0.$$

The solutions to this equation are:

$$\lambda = \frac{\sqrt{8} \pm \sqrt{8 - 4 \cdot 1}}{2} = \frac{2\sqrt{2} \pm 2}{2} = \sqrt{2} \pm 1.$$

In other words, $\lambda_1 = \sqrt{2} + 1$ and $\lambda_2 = \sqrt{2} - 1$. The solution to the homogeneous equation has the form $\mathbf{x} = K_1 \mathbf{v}_1 e^{\lambda_1 t} + K_2 \mathbf{v}_2 e^{\lambda_2 t}$. To determine \mathbf{v}_1 and \mathbf{v}_2 , we assume without loss of generality

$\mathbf{v}_1 = \begin{bmatrix} 1 \\ v_1 \end{bmatrix}$ and $\mathbf{v}_2 = \begin{bmatrix} 1 \\ v_2 \end{bmatrix}$. These eigenvectors must satisfy:

$$\begin{aligned} \begin{bmatrix} \lambda_1 & -1 \\ 1 & \lambda_1 - \sqrt{8} \end{bmatrix} \begin{bmatrix} 1 \\ v_1 \end{bmatrix} &= \begin{bmatrix} 0 \\ 0 \end{bmatrix}, \\ \begin{bmatrix} \lambda_2 & -1 \\ 1 & \lambda_2 - \sqrt{8} \end{bmatrix} \begin{bmatrix} 1 \\ v_2 \end{bmatrix} &= \begin{bmatrix} 0 \\ 0 \end{bmatrix}. \end{aligned}$$

From here, it is easy to see that $v_1 = \lambda_1$ and $v_2 = \lambda_2$ and then:

$$x_1(t) = K_1 e^{(\sqrt{2}+1)t} + K_2 e^{(\sqrt{2}-1)t},$$

$$x_2(t) = K_1(\sqrt{2} + 1)e^{(\sqrt{2}+1)t} + K_2(\sqrt{2} - 1)e^{(\sqrt{2}-1)t}.$$

The initial conditions determine the constants K_1, K_2 as follows:

$$C = x_1(0) = K_1 + K_2$$

$$D = x_2(0) = K_1(\sqrt{2} + 1) + K_2(\sqrt{2} - 1).$$

Solving for K_1 and K_2 , we get:

$$K_1 = \frac{C(1 - \sqrt{2}) + D}{2},$$

$$K_2 = \frac{C(\sqrt{2} + 1) - D}{2}.$$

The solutions do not satisfy the condition of BIBO stability because the exponentials in $x_1(t)$ and $x_2(t)$ grow unbounded as t tends to infinity.

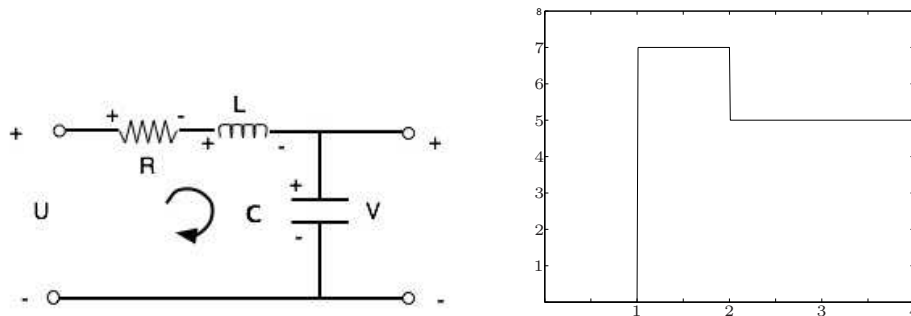


Figure 1: Circuit diagram for Problem 1 (left) and input signal for Problem 2 (right)